

Week 12

1. Write a program to implement Digital Logic Gates – AND, OR, NOT, EXOR

Program(

and): def

AND(a,b)

: if

a==1 and

b==1:

return

True

else:

return

False

print(AND(1,1),"=AND(1,1)")

print(AND(0,0),"=AND(0,0)")

print(AND(1,0),"=AND(1,0)")

print(AND(0,1),"=AND(0,1)") **output:**

True =AND(1,1)

False =AND(0,0)

False =AND(1,0)

False =AND(0,1)

Progra

m(or):

def

OR(a,b):

if a==1

or b==1:

return

True

else:

return

False

```
print(OR(1,1),"=
OR(1,1)")
print(OR(0,0),"=
OR(0,0)")
print(OR(1,0),"=
OR(1,0)")
print(OR(0,1),"=
OR(0,1)")
output: True
=OR(1,1)
False =OR(0,0)
True =OR(1,0)
True =OR(0,1)
```

Prog

ram(

not):

```
def
NOT
(a):
if
a==1
:
    return False
else:
    return True
print(NOT(1),"
=NOT(1)")
print(NOT(0),"
=NOT(0)")
output: False
=NOT(1)
True =NOT(0)
```

Program(

EX-OR):

```
def
XOR_gat
```

```

e(a, b):
if a != b:
return 1
else:
    return 0
print("XOR Gate:",
XOR_gate(5,5)) output:
XOR Gate: 0

```

2. Write a program to implement Half Adder, Full Adder, and Parallel Adder.

Program(Ha lf Adder):

```

def
XOR(a,b):
if a!=b:
return 1
else:

return
0 def
AND(
a,b):
if
a==b:
return
1
else:
    return 0 def
half_adder(a,b):
sum=XOR(a,b)
carry=AND(a,b)
return sum,carry
sum,carry=half_
adder(0,0)
print(sum,carry)
sum,carry=half_
adder(0,1)
print(sum,carry)
sum,carry=half_
adder(1,0)

```

```

print(sum,carry)
sum,carry=half_
adder(1,1)
print(sum,carry)

```

output: 0 1

1 0

1 0

0 1

Program(full adder): def

```
half_adder(a,b):    sum=a^b
```

```
carry = a and b    return
```

```
carry,sum def
```

```
full_adder(carry_in,a,b):
```

```
carry1,sum1=half_adder(car
ry_in,a)
```

```
carry2,sum=half_adder(sum
1,b)    carry=carry1 or
```

```
carry2    return carry,sum
```

```
carry,sum=full_adder(0,0,0)
```

```
print(sum,carry)
```

```
carry,sum=full_adder(0,0,1)
```

```
print(sum,carry)
```

```
carry,sum=full_adder(0,1,0)
```

```
print(sum,carry)
```

```
carry,sum=full_adder(0,1,1)
```

```
print(sum,carry)
```

```
carry,sum=full_adder(1,0,0)
```

```
print(sum,carry)
```

```
carry,sum=full_adder(1,0,1)
```

```
print(sum,carry)
```

```
carry,sum=full_adder(1,1,0)
```

```
print(sum,carry)
```

```
carry,sum=full_adder(1,1,1)
```

```
print(sum,carry) output: 0 0
```

1 0

1 0

0

0

0

1

Error! Bookmark not defined.

Error! Bookmark not defined.

Error! Bookmark not defined.

Error! Bookmark not defined.

1 0

Parallel **Adder:**

```
#
# To use these functions, you can run python and then
import like - # from binary_adder import *
#
# These methods carry out binary addition via
'digital logic' # This is really what happens at the
logic circuit level.
# So, this is a pretty abstract use of programming to illustrate
# what happens on silicon using code many, many, levels
above that! #

# A binary half adder -- performing addition only using logic
operators,
# A half adder simply adds two bits and outputs a sum and carry
# def half_adder(a,
b):    # ^ is logical
xor in python
sum = a ^ b
carry = a and b
return carry,sum

# A binary full adder
# The full adder can add 3 bits (can handle an incoming carry)
# Also returns a sum and carry
# def full_adder(carry_in, a,
b):    carry1,sum1 =
half_adder(carry_in,a)
carry2,sum =
half_adder(sum1,b)    carry
= carry1 or carry2    return
carry,sum

# This method virtually chains together binary full adders
in order # to add binary numbers of arbitrary size.
#
```

```

# a and b are expected to be strings representing
binary integers. # # def binary_adder(a,b):
    an
    =
    len(a)
    bn =
    len(b)

    # Convert strings to list of bits -- very functional syntax here
    al = list(int(x,2) for x in list(a))
    bl = list(int(x,2) for x in list(b))

    # Pad smaller list
    with 0's    dif = an -
    bn
    # more digits
    in a than b    if
    dif > 0:        for i
    in range(dif):
    bl.insert(0,0)
    else:          for i in
    range(abs(dif)):
        al.insert(0,0)

    print(al)
    print(bl)

    result
    = []
    carry =
    0
    # Iterate through list right to left, calling full_adder each time and
    # inserting the sum each time
    for i in range(len(al)-1,-1,-1):
    carry,sum =
    full_adder(carry,al[i],bl[i])
    result.insert(0,sum)    print
    (result)
    result.insert(0,carry)

```

```

        return ".join(str(x) for x in result)

def
test_binary_adder(a,b)
:   result =
binary_adder(a,b)
print(result)
    if (int(a,2) + int(b,2)) == int(result,2):
        print("Woo hoo! It
works")    else:
        print("FAIL!!")
        print(str(int(a,2)) + " + " + str(int(b,2)) + " = " + str(int(result,2)))
test_binary_adder('11111','11111')

```

Output:

```

[1, 1, 1, 1, 1]
[1, 1, 1, 1, 1]
[0]
[1, 0]
[1, 1, 0]
[1, 1, 1, 0]
[1, 1, 1, 1, 0]
111110
Woo hoo! It works
31 + 31 = 62

```